

(Following Paper ID and Roll No. to be filled in your Answer Books)

Paper ID : 2289954

Roll No.

| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|
| | | | | | | | | | |
|--|--|--|--|--|--|--|--|--|--|

B.TECH.

Regular Theory Examination (Odd Sem - III),2016-17

DIGITAL LOGIC DESIGN

Time : 3 Hours

Max. Marks : 100

Note: Attempt All sections. If require any missing data: then choose suitably.

Section - A

1. Attempt all questions in brief. (10×2=20)
- Perform 2's complement subtraction of 010110-100101.
 - What is the feature of gray code?
 - Write the logic equation and draw the internal logic diagram for a 4 to 1 mux.
 - What is a priority encoder?
 - List the major differences between PLA and PAL.

- f) Define a Bus. What are the different types of buses?
- g) Give the comparison between combinational circuits and sequential circuits.
- h) What are the different types of flip-flop?
- i) Give the comparison between synchronous & asynchronous sequential circuits.
- j) When does race condition occur?

Section - B

2. Attempt any three of the following: (3×10=30)

- a) Reduce the Boolean function using k-map technique and implement using gates
 $f(w, x, y, z) = \sum m(0, 1, 4, 8, 9, 10)$ which has the don't cares condition $d(w, x, y, z) = \sum m(2, 11)$
- b) Implement the following multiple output combinational logic circuit using a 3 to 8 decoder.
 - i) $f_1 = \sum m(1, 2, 3, 5, 7)$

- ii) $f_2 = \sum m(0, 3, 6)$
- iii) $f_3 = \sum m(0, 2, 4, 6)$
- c) What is Ram? Explain the different types of RAM in detail.
- d) Realize
 - i) A JK flip flop using SR flip flop.
 - ii) A SR flip flop using NAND gates and explain its operation.

Section - C

3 Attempt any one part of the following (1×10=10)

- a) Detect and correct error (if any) in the following received even parity Hamming code word 00111101010.
- b) Minimize the given Boolean function using Quine Mc Clusky method
 $f(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 8, 9, 11, 15)$ and implement the simplified function using NOR gates only.

4. Attempt any one part of the following (1×10=10)

- a) i) Obtain the simplified Boolean expression for the output F and G in terms of the input variables in the circuit of fig. 1

 


Fig. 1

- ii) Implement the full adder and full subtractor using decoder.
- b) i) Design a combinational circuit that compares the magnitude of two 3 bit numbers and its output indicates whether $A > B$, $A = B$, $A < B$.
- ii) Construct a BCD to excess 3 code converter with a 4 bit adder. What must be done to change the circuit to an excess 3 to BCD code converter?

5. Attempt any one part of the following (1×10=10)

- a) Design a combinational circuit using a ROM. The circuit accepts a three-bit number and outputs a binary number equal to the square of the input number.

- b) Draw a PLA circuit to implement the functions

$$f_1 = A'B + AC' + A'BC', f_2 = (AC + AB + BC)', f_3 = BC + AC + A'BC'$$

6. Attempt any one part of the following (1×10=10)

- a) A sequential circuit has three flip flop A,B and C; one input x in and one output y out. The state diagram is shown in fig2. The circuit is to be designed by treating the unused states as don't-care conditions. Use T flip flop in the design.

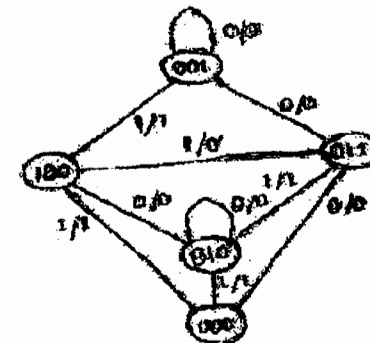


Fig. 2

- b) Design a 4 bit binary synchronous counter with D flips flop.

7. Attempt any one part of the following (1×10=10)

- a) Derive the transition table for the asynchronous sequential circuit shown in fig.3 determine the sequence of internal states $Y_1 Y_2$ for the following sequence of input $X_1 X_2$: 00,10,11,01,11,10,00.

 


Fig. 3

- b) An asynchronous sequential circuit is described by the excitation function

$$Y = x_1 x_2' + (x_1 + x_2')y \text{ and } z = y$$

- i) Draw the logic diagram of the circuit
 ii) Drive the transition table and output map.
