



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 131406

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

**(SEM. IV) THEORY EXAMINATION, 2014-15
ELECTRONIC CIRCUITS**

Time : 3 Hours]

[Total Marks : 100

Note: (1) Attempt all questions.

(2) All questions carry equal marks:

1 Attempt **any four** parts of the following:- **5×4=20**

- (a) Draw the circuit diagram of difference amplifier using OP-AMP and calculate the differential gain (A_d) and differential input resistance(R_{id}).
- (b) For the circuit in Fig.(1) calculate the values of v_1 , i_1, i_2, v_0, i_L and i_o . Also calculate the voltage gain, current gain and power gain.

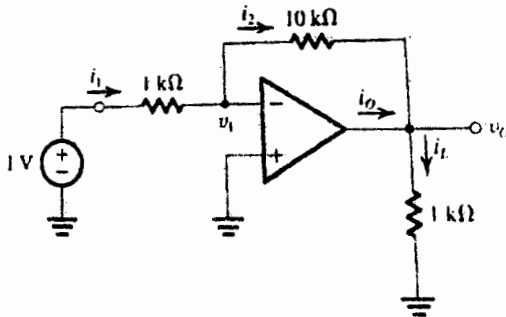


Fig.(1)

- (c) Explain how the performance of an OP-AMP is affected by the open loop gain of an amplifier.
- (d) Explain the effect of finite open loop gain and bandwidth on the circuit performance. And calculate the frequency response of closed loop inverting amplifier.
- (e) An inverting amplifier with nominal gain of $-20V/V$ employs an op-amp having a dc gain of 10^4 and a unity gain frequency of 10^6Hz . What is the 3-dB frequency $f_{3\text{dB}}$ of the closed loop amplifier? What is the gain at $0.1 f_{3\text{dB}}$ and at $10f_{3\text{dB}}$.
- (f) (i) Describe the terms Unity-gain Bandwidth and Full-power Bandwidth.
- (ii) For an op-amp having a slew rate of $60\text{ V}/\mu\text{s}$, what is the highest frequency at which a 20-V peak to peak sine wave can be produced at the output.

2 Attempt any four parts of the following:- $5 \times 4 = 20$

- (a) Derive the $i_D - V_{ds}$ relationship for NMOS working in saturation region.

- (b) Explain the need of biasing. Also explain the merits and demerits of the various biasing techniques used in MOSFET.
- (c) Consider the FET amplifier of Fig.(2) for the case $V_t = 2\text{V}$, $kn'(W/L) = 1\text{mA}/\text{V}^2$, $V_{GS} = 4\text{V}$, $V_{DD} = 10\text{V}$ and $R_D = 3.6\text{K}\Omega$.

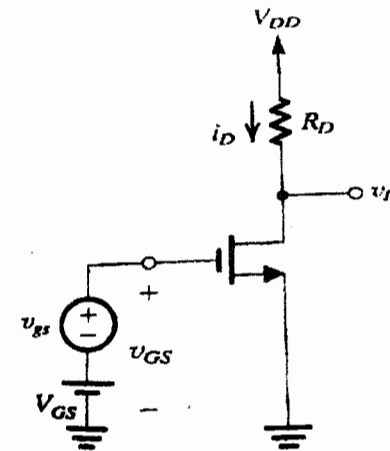


Fig.(2)

- (i) Find the dc quantities I_D and V_D .
- (ii) Calculate the value of g_m at the bias point.
- (iii) Calculate the value of voltage gain.
- (iv) If the MOSFET has $\lambda = 0.001\text{V}^{-1}$, find r_o at the bias point and calculate the voltage gain.

- (d) Calculate the MOSFET Unity –Gain Frequency (F_T) with the help of MOSFET high frequency model.
- (e) In the circuit of Fig.(3) let $R_G = 10M\Omega$, $R_D = 10K\Omega$, and $V_{DD} = 10V$. Find the value of V_D and V_G for $V_t = 1V$ and $kn' (W/L) = 0.5m A/V^2$.

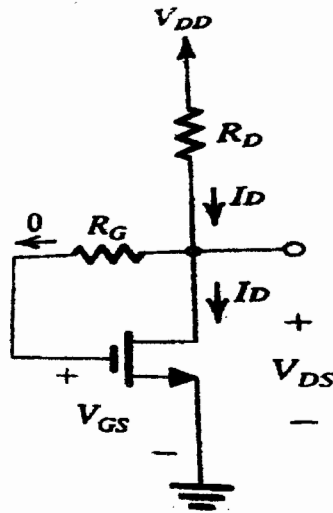


Fig. (3)

- (f) Calculate the overall gain $G_v = V_o/V_{sig}$, input resistance and output resistance for a Common Source Amplifier.

3 Attempt any two parts of the following: $10 \times 2 = 20$

- (a) Explain the working of BJT as an amplifier and as a switch with the help of neat diagram and necessary equations. Also calculate the amplifier gain.
- (b) Calculate the voltage gain for the circuit given in Fig.(4). Assume $\beta = 100$.

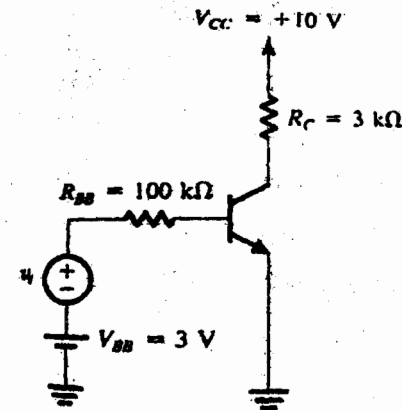


Fig.(4)

- (c) Explain the effect of each capacitor of a CE amplifier with the gain frequency curve. Also discuss the low frequency response of a CE amplifier.